

[Introduction to Computer Architecture'21] Tutorial 2

Content:

Exercise 1: Construct a 4x16 decoder from 2x4 decoders only.

Exercise 2: Construct a 8x1 multiplexer from 4x1 multiplexers and one 2x1 multiplexer only.



Exercise 3 - Hands on: Implement a full adder using suitable NAND decoder only.

[Introduction to Computer Architecture'21] Tutorial 2

Exercise 1: Construct a 4x16 decoder from 2x4 decoders only.

4x16 Decoder:


A	B	C	D	I0	I1	I2	I3	I4	I5	I6	I7	I8	I9	I10	I...
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	..
0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	..
0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	..

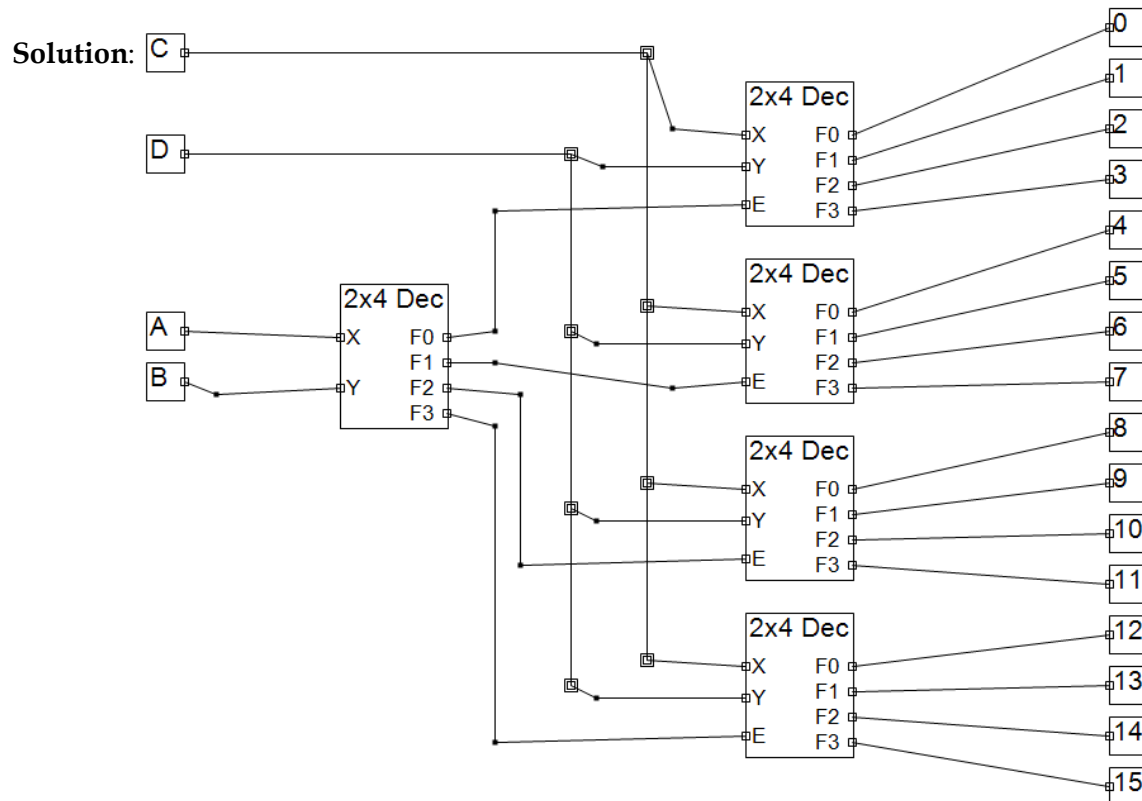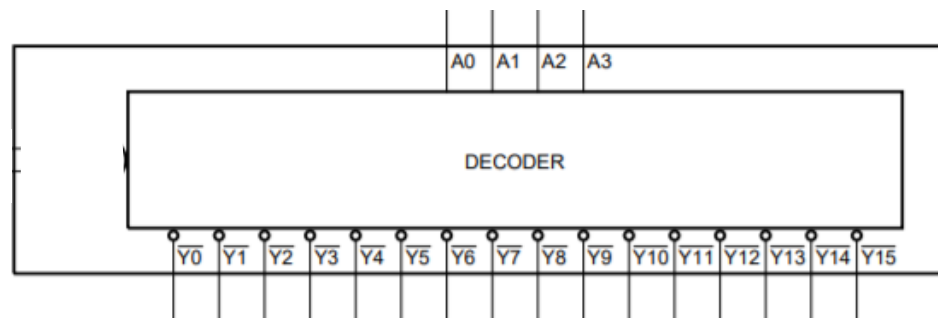

[Introduction to Computer Architecture'21] Tutorial 2

Construct a 8x1 multiplexer from 4x1 multiplexers and one 2x1 multiplexer only.

Solution:

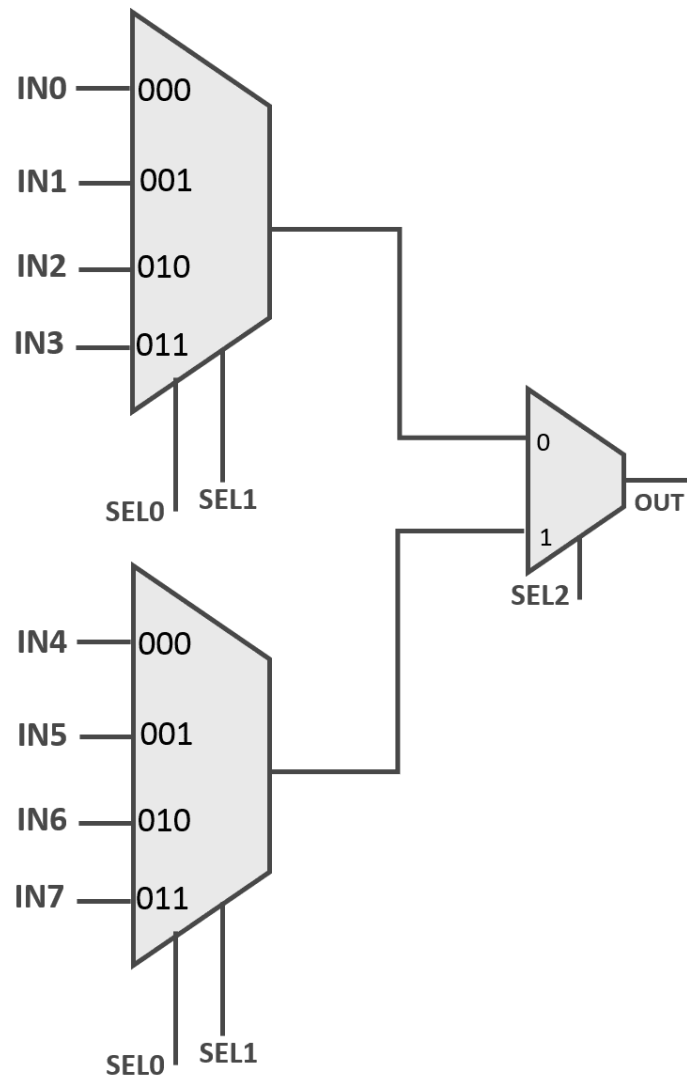


[Introduction to Computer Architecture'21] Tutorial 2

Exercise 3 – Hands on: Implement a full adder using suitable NAND decoder only.

Hint(s):

1- Full Adder Design:

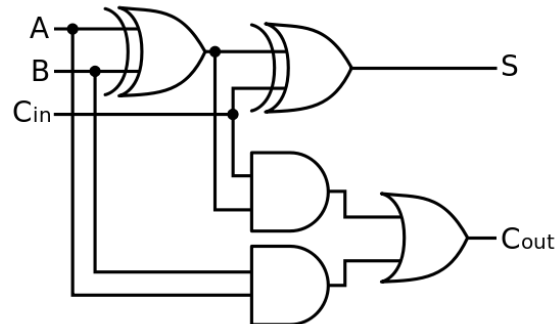

2- Full Adder Truth Table:

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Verilog + ZYBO Z7 board Help:

- Check this link for Verilog syntax:
<https://www.nandland.com/verilog/tutorials/index.html>
- Check this link for ZYBO Z7 board info.:
<https://digilent.com/reference/programmable-logic/zybo/start>

If you need any help regarding anything about the course, ask:

- Engr. Ahmad M. Abdel-Hafeez: akassem@nu.edu.eg
- Engr. Mohammad Rady: mrady@nu.edu.eg