 


## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

**Question 1:** Analyze the following circuit.



**\*\*Hit:**  $F(A, B, C) = \sum (1, 2, 7)$  Means that the function output will be 1 at combination  $(1)_{10} = (001)_2$  and combination  $(2)_{10} = (010)_2$  and so on. Otherwise, the function output will be 0.

**Requirement(s):**

Answer the following question(s):

**Build the truth table**

- 1- # inputs = 3 (X, Y, Z)
- 2- # outputs = 1 (F)

X	Y	Z	D (X, Y, Z) I0	B (X, Y, Z) I1	$X \wedge Z$	F (X, Y, Z)
0	0	0	0	0	0	0
0	0	1	1	1	1	1
0	1	0	1	1	0	1
0	1	1	0	1	1	1
1	0	0	1	0	1	0
1	0	1	0	0	0	0
1	1	0	0	0	1	0
1	1	1	1	1	0	1

1- The output D (X, Y, Z) =  $\sum (1, 2, 4, 7)$  [produces 1 at 1, 2, 4 and 7]

2- The output B (X, Y, Z) =  $\sum (1, 2, 3, 7)$  [produces 1 at 1, 2, 3 and 7]

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

**Question 2:** Implement the following Function  $F(W, X, Y, Z)$  using 4x1 multiplexer

$$F(W, X, Y, Z) = \sum (2, 3, 5, 7, 12, 13, 14, 15)$$

**Requirement(s):**

Answer the following question(s):

Means that the function output will be 1 at combination  $(1)_{10} = (0001)_2$  and combination  $(2)_{10} = (0010)_2$  and so on. Otherwise, the function output will be 0.


**Truth Table:**

W	X	Y	Z	F(W, X, Y, Z)	
0	0	0	0	0	I0
0	0	0	1	0	
0	0	1	0	1	
0	0	1	1	1	
0	1	0	0	0	I1
0	1	0	1	1	
0	1	1	0	0	
0	1	1	1	1	
1	0	0	0	0	I2
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	0	
1	1	0	0	1	I3
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	1	

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution


---

Design this circuit:

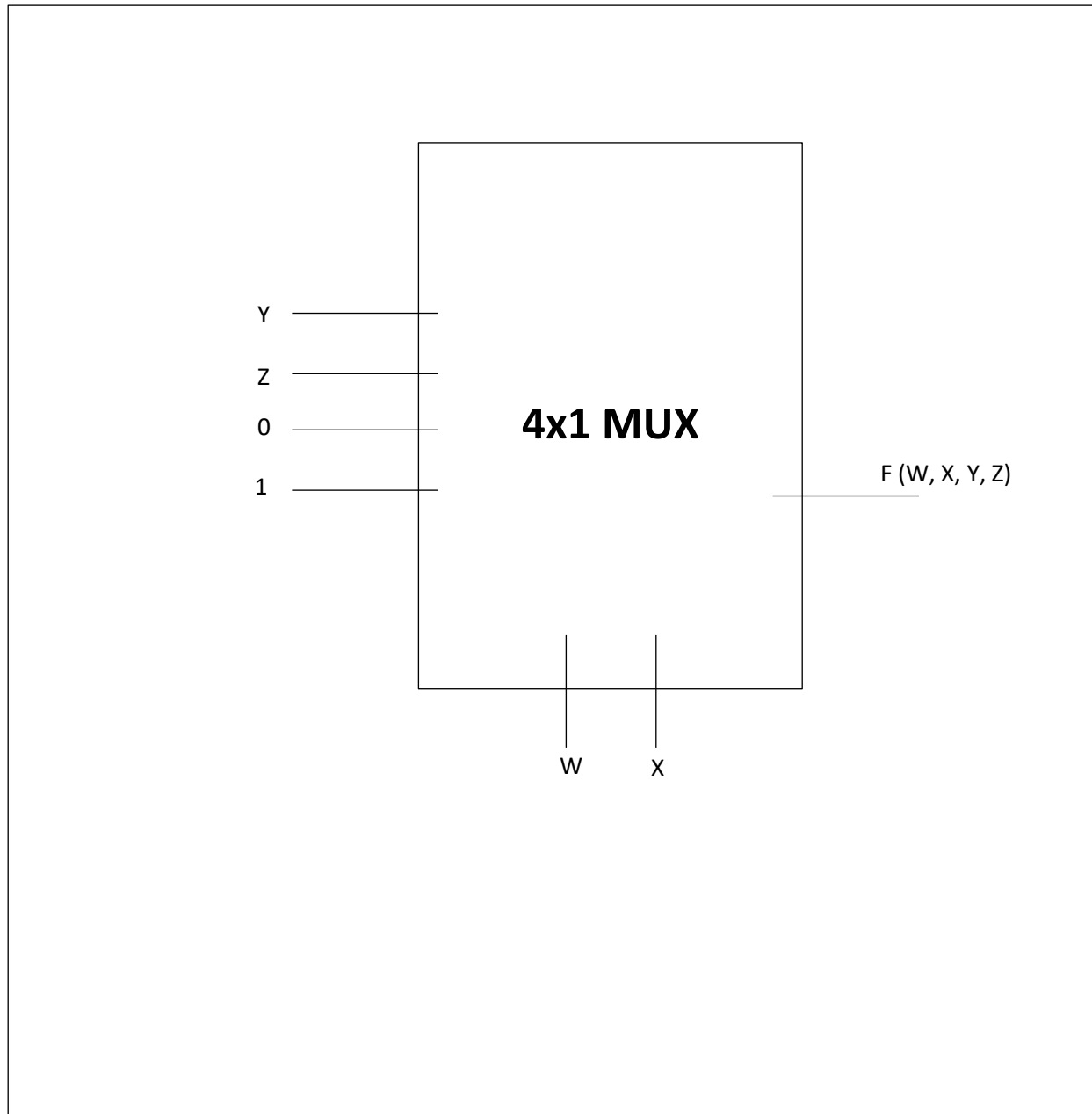

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

 **Question 3:** Analyze the following circuit, then redesign with suitable Multiplexer.



**Requirement(s):**

Answer the following question(s):

**Truth Table:**


X	Y	Z	Decoder 1				Decoder 2				F (X, Y, Z)
			3	2	1	0	7	6	5	4	
0	0	0	0	0	0	1	0	0	0	1	1
0	0	1	0	0	1	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	1	0	0
0	1	1	0	0	1	0	0	0	1	0	0
1	0	0	0	1	0	0	0	1	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	1	0	0	1	0	0	0	0
1	1	1	1	0	0	0	1	0	0	0	1

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

---

Re-Design this circuit:

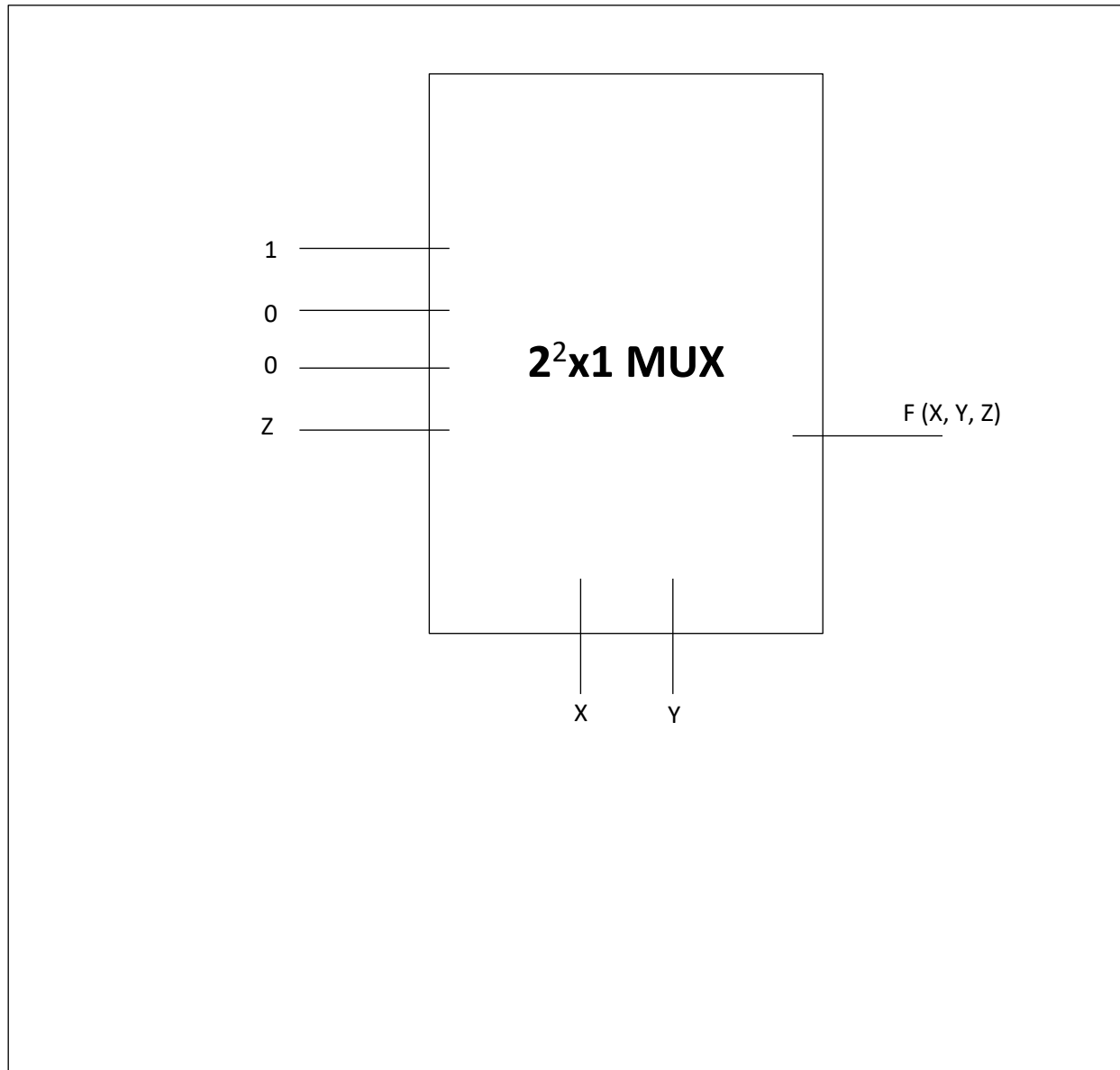**\*\*Hint:** *Suitable Mux = # of inputs - 1*



## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

**Question 4:** Design a counter that counts the following sequence 3, 1, 2 using D flip flops.

**Requirement(s):**


Answer the following question(s):

# External Inputs = 0

# External Outputs = 0

# Flip-Flops = 2 (1 for each bit)

**State Diagram:**

 

**State Table:**

$A_n$	$B_n$	$D_A$	$D_B$	$A_{n+1}$	$B_{n+1}$
0	0	X	X	X	X
0	1	1	0	1	0
1	0	1	1	1	1
1	1	0	1	0	1


$$D_A = A_{n+1} = A_n \wedge B_n$$

$$D_B = B_{n+1} = A_n$$

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution


---

Design this circuit:

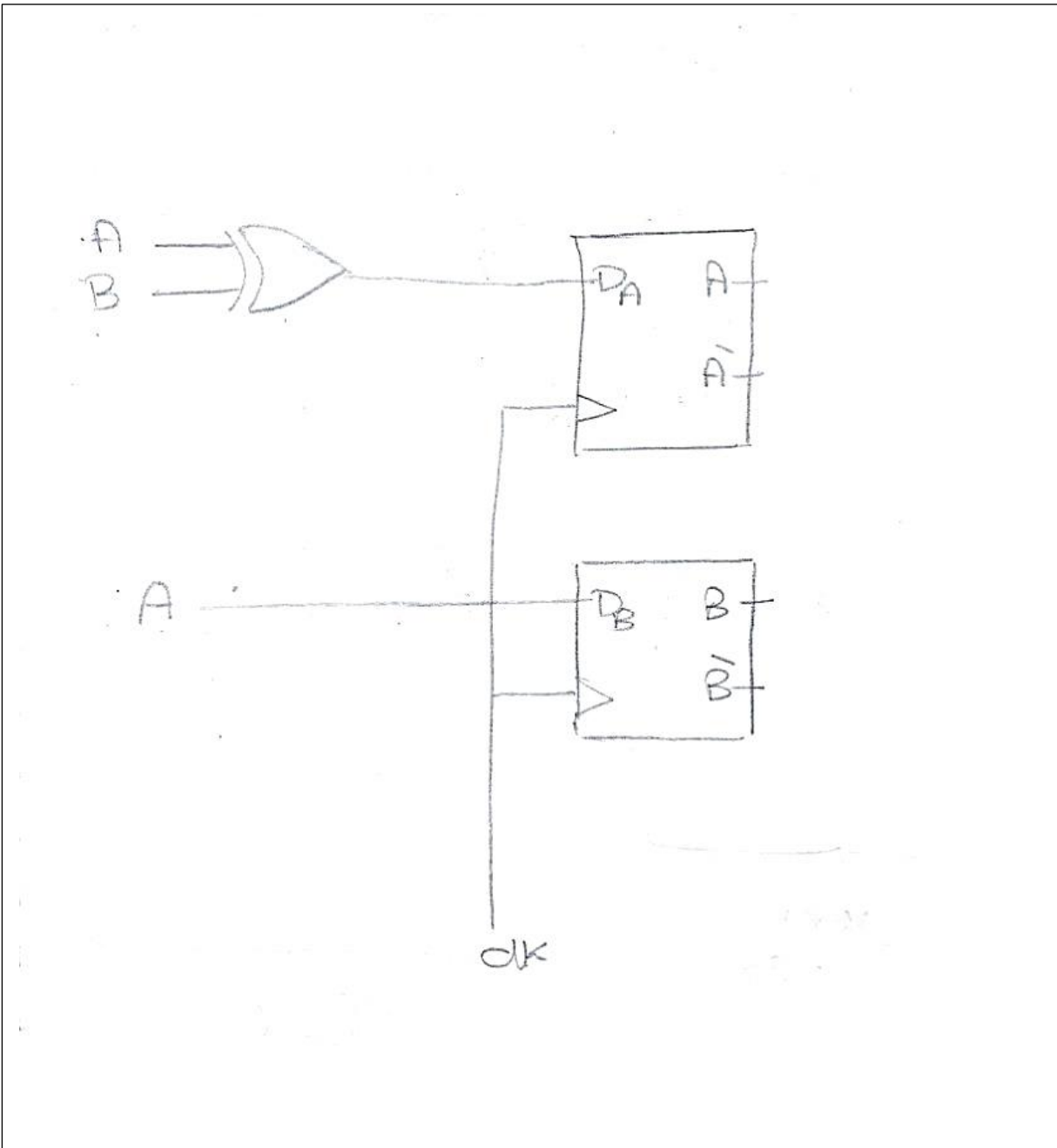

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

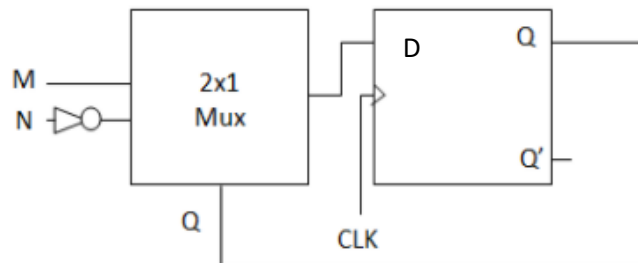**Question 5:** Analyze the following sequential circuit for M N flipflop and then find its state and characteristic tables.



**Requirement(s):**

Answer the following question(s):

**State Table:**

M	N	$Q_n$	$Q_{n+1} (D)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

**Characteristic Table:**


M	N	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$Q_n'$



## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution


---

State Diagram:

 

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

 **Question 6:** Design a sequential circuit using D flip flops according to the following state diagram.



**Requirement(s):**

Answer the following question(s):

- 1- # Of external inputs = 1
- 2- # Of external outputs = 2
- 3- # Of flip-flops = 2
- 4- # Of total inputs = 3

**State Table:**

X	A <sub>n</sub>	B <sub>n</sub>	A <sub>n+1</sub> (D <sub>A</sub> )	B <sub>n+1</sub> (D <sub>B</sub> )	O1	O0
0	0	0	0	1	0	0
0	0	1	1	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	0	1
1	0	0	1	1	1	0
1	0	1	0	0	1	1
1	1	0	0	1	1	0
1	1	1	1	0	1	1

$$D_A = A_{n+1} = X \wedge A_n \wedge B_n$$


$$O1 = X$$

$$D_B = B_{n+1} = B_n'$$

$$O0 = B_n$$


## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

Design:

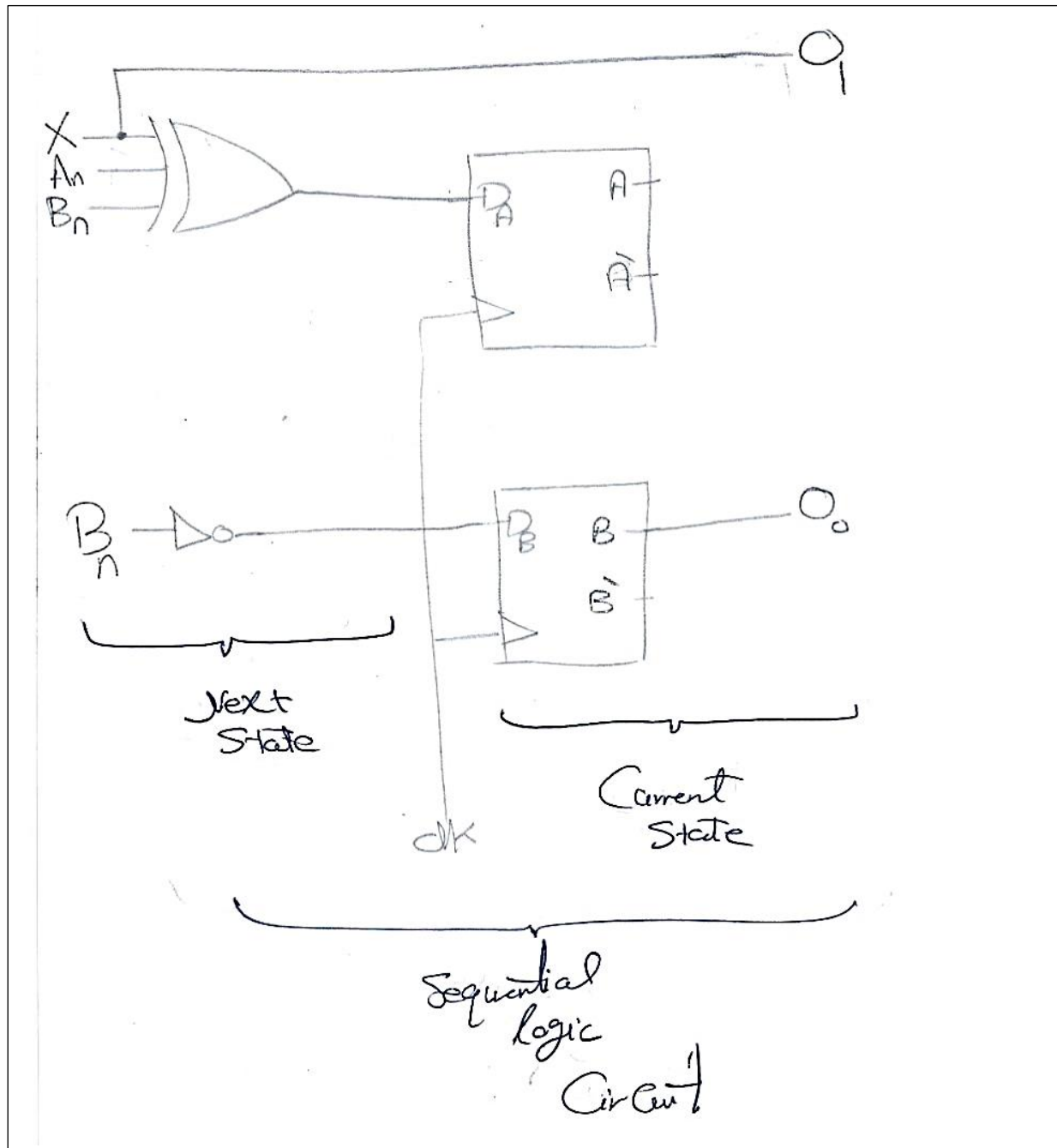

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

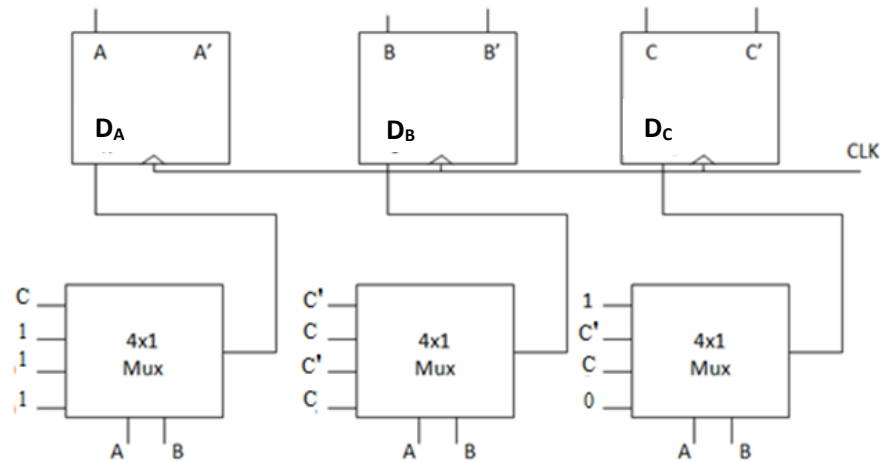**Question 7:** Analyze the following counter circuit.



**Requirement(s):**

Answer the following question(s):

# Of external inputs = 0

# Of external outputs = 0

# Of flip-flops = 3

# Of total outputs = 6

**State Table:**

$A_n$	$B_n$	$C_n$	$A_{n+1} (D_A)$	$B_{n+1} (D_B)$	$C_{n+1} (D_C)$
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	1	1	0
1	0	1	1	0	1
1	1	0	1	0	0
1	1	1	1	1	0

## [Introduction to Computer Architecture'21] Combinational and Sequential Circuits Revision 1 - solution

---

State Diagram:

