

[Introduction to Computer Architecture'21] Lab: Assignment 1

Description: Implement 2-bit Adder using Verilog with ZYBO Z7 board.

Requirement(s):

- 1- Create Module to implement 2-bit Adder.
- 2- Create Module to run 2-bit Adder on ZYBO Z7 board.

Deadline: Next lab (week 2).

Grade: [0, 10] depend on your work.

Verilog + ZYBO Z7 board Help:

- Check this link for Verilog syntax:
<https://www.nandland.com/verilog/tutorials/index.html>
- Check this link for ZYBO Z7 board info.:
<https://digilent.com/reference/programmable-logic/zybo/start>

If you need any help regarding anything about the course, ask:

- Engr. Ahmad M. Abdel-Hafeez: akassem@nu.edu.eg
- Engr. Mohammad Rady: mrady@nu.edu.eg

[Introduction to Computer Architecture'21] Lab: Assignment 1

Hint(s):

1- Check the below truth table

| A | | B | | SUM |
|----|----|----|----|-----|
| A0 | A1 | A2 | A3 | |
| 0 | 0 | 0 | 0 | 00 |
| 0 | 0 | 0 | 1 | 01 |
| 0 | 0 | 1 | 0 | 10 |
| 0 | 0 | 1 | 1 | 11 |
| 0 | 1 | 0 | 0 | 01 |
| 0 | 1 | 0 | 1 | 10 |
| 0 | 1 | 1 | 0 | 11 |
| 0 | 1 | 1 | 1 | 100 |
| 1 | 0 | 0 | 0 | 10 |
| 1 | 0 | 0 | 1 | 11 |
| 1 | 0 | 1 | 0 | 100 |
| 1 | 0 | 1 | 1 | 101 |
| 1 | 1 | 0 | 0 | 11 |
| 1 | 1 | 0 | 1 | 100 |
| 1 | 1 | 1 | 0 | 101 |
| 1 | 1 | 1 | 1 | 110 |

2- Check the below design

