 


Implement n-bit full ALU. (10 points)

Description: The ALU performs simple addition, subtraction, multiplication, division, and logic operations, such as OR and AND. The memory stores the program's instructions and data.


Main module should be called "ALU"





ALU Functional Specifications:

ALU OPCODE	Function
0000	AND
0001	OR
0010	ADD
0110	SUB

 

1-bit ALU Process



Testbench [Main] should look as follows:

```
module Main();

reg [31:0] data1;

reg [31:0] data2;

reg [3:0] aluop;

reg cin;

wire [31:0] dataout;

wire cflag;

wire zflag;

wire oflag;
```

Delivery Method: on Moodle [only one in each team can submit the team project folder]

Grading Schema:

Code structure	2 (points)
WAVE window	2 (points)
RTL Design	2 (points)
Test 1	0.25 (point)
Test 2	0.25 (point)
Test 3	0.25 (point)
Test 4	1 (point)
Test 5	0.25 (point)
Test 6	1 (point)
Test 7	1 (point)
Total	10 (points)

Deadline: Friday November 19, 2021 @ 11:59 PM



Deliverables:

You should submit the following file(s) on Moodle:

- 1. ZIP file for Lab Project Phase 1 (File name must be of the following format:
 - CA21_LP1_Student1ID_ Student2ID_ Student3ID.zip) contains the following file(s):
 - a. Each module you're created [.v].
 - b. Screenshot of the WAVE window [7 tests].
 - c. ALU Schematic [RTL Design].
 - d. Document file [.pdf] contains your work in each module.
 - e. Text file contains the team's info. (*Team ID*, *Team Names and Team IDs*).

upload the below files on Moodle:

Rules:

- 1. Each team consists of *3 students* at most.
- 2. Any submissions after the deadline are not acceptable.
- 3. Important Plagiarism Notice:
 - a. Deliverables based on other students' solutions lead to rejection of BOTH deliverables.
 - b. Examples of plagiarism (but not limited to) copying (partial) code from other students, open-source software (or Internet in general), tutors, etc.

Search before ask

Verilog + ZYBO Z7 board Help:

- Check this link for Verilog syntax:
 https://www.nandland.com/verilog/tutorials/index.html
- Check this link for ZYBO Z7 board info.: https://digilent.com/reference/programmable-logic/zybo/start

If you need any help regarding anything about the course, ask:

- Engr. Ahmad M. Abdel-Hafeez: akassem@nu.edu.eg
- Engr. Mohammad Rady: mrady@nu.edu.eg



Test before submitting:

Test #1:

Type	Name	Value
input	data1	110000000000000000000000000000000000000
input	data2	101000000000000000000000000000000000000
input	aluop	0000
ouput	dataout	100000000000000000000000000000000000000
output	zflag	0

Test #2:

Type	Name	Value
input	data1	110000000000000000000000000000000000000
input	data2	101000000000000000000000000000000000000
input	aluop	0001
ouput	dataout	111000000000000000000000000000000000000
output	zflag	0

Test #3:

Type	Name	Value
input	data1	011100000000000000000000000000000000000
input	data2	011000000000000000000000000000000000000
input	aluop	0010
ouput	dataout	110100000000000000000000000000000000000
output	zflag	0
output	oflag	1
output	cflag	0



Test #4:

Type	Name	Value
input	data1	111100000000000000000000000000000000000
input	data2	000100000000000000000000000000000000000
input	aluop	0010
ouput	dataout	000000000000000000000000000000000000000
output	zflag	1
output	oflag	0
output	cflag	1

Test #5:

Type	Name	Value
input	data1	0000000000000000000000000000111
input	data2	000000000000000000000000000000000000000
input	aluop	0110
input	cin	1
ouput	dataout	000000000000000000000000000000000000000
output	zflag	0
output	oflag	0
output	cflag	1

Test #6:

Type	Name	Value
input	data1	00000000000000000000000000000000110
input	data2	0000000000000000000000000000111
input	aluop	0110
input	cin	1
ouput	dataout	111111111111111111111111111111111111111
output	zflag	0
output	oflag	0
output	cflag	0



Test #7:

Type	Name	Value
input	data1	1111111111111111111111111000
input	data2	000000000000000000000000000000000000000
input	aluop	0110
input	cin	1
ouput	dataout	111111111111111111111111111111111111111
output	zflag	0
output	oflag	1
output	cflag	1